

## Equations

1.  $P = \frac{dW}{dt} = IV$
  2.  $I = \frac{dq}{dt}$
  3.  $V = \frac{W}{q}$
  4.  $R = \frac{\rho L}{A}$
  5. Ohm's Law:  $V = IR$
  6. Coulomb's Law:  $\vec{F} = \frac{1}{4\pi\epsilon_0} \frac{q_1 q_2}{r^2} \hat{r}$
  7. Kirchhoff's Voltage Law:  $\sum V_i = 0$  (around a closed loop)
  8. Kirchhoff's Current Law:  $\sum I_i = 0$  (going into a node)
  9. Conductance:  $G = \frac{1}{R}$
  10. Equivalent resistance:  $R_{eq} = \frac{V_{test}}{I_{test}}$
  11. Series capacitance:  $\frac{1}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$
  12. Parallel capacitance:  $C_{total} = C_1 + C_2 + \dots$
  13. Series inductor:  $L_{total} = L_1 + L_2 + \dots$
  14. Parallel inductor:  $\frac{1}{L_{total}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots$
  15.  $I_{cap} = C \frac{dV}{dt}$
  16.  $V_{ind} = L \frac{dI}{dt}$
  17. Energy stored in capacitor:  $\frac{1}{2} CV^2$
  18. Energy stored in inductor:  $\frac{1}{2} LI^2$
  19. Voltage in RC circuit:  $v_c(\infty) + (v_c(t_0) - v_c(\infty)) e^{(\frac{-1}{RC})(t-t_0)} = x(t_0) e^{\lambda(t-t_0)}$  (if  $v_c(\infty) = 0$ )
  20. Current in RL circuit:  $I_L(\infty) + (I_L(t_0) - I_L(\infty)) e^{(\frac{-R}{L})(t-t_0)}$
  21. Impedance of a capacitor:  $\frac{-j}{\omega C}$
  22. Impedance of an inductor:  $j\omega L$
  23. Equivalent impedance for impedances in series:  $Z_{eq} = \sum_i^n Z_i$
  24. Equivalent impedance for impedances in parallel:  $\frac{1}{Z_{eq}} = \sum_i^n \frac{1}{Z_i}$
  25. Maximum power extracted by a load in DC circuits:  $\frac{V_{th}^2}{4R_{th}}$
  26. Maximum power extracted by a load in AC circuits:  $\frac{|\tilde{V}_{th}|^2}{8R_{th}}$
- ( $R_{eq}$ ) Turn off all independent sources (dependent sources remain unchanged) and calculate the resulting resistance at the desired port. Notice that you may have to apply the i-v test if resistors cannot be combined through series and parallel connections, or if the circuit includes dependent sources.
- ( $V_{th}$ ) Leave the desired port open-circuited (i.e. no load connected) and find the voltage across it.
- ( $I_N$ ) Short-circuit the desired port (i.e. connect a short circuit across the port) and find the current through it.