

## Equations

1.  $P = \frac{dW}{dt} = IV$
  2.  $I = \frac{dq}{dt}$
  3.  $V = \frac{W}{q}$
  4.  $R = \frac{\rho L}{A}$
  5. Ohm's Law:  $V = IR$
  6. Coulomb's Law:  $\vec{F} = \frac{1}{4\pi\epsilon_0} \frac{q_1 q_2}{r^2} \hat{r}$
  7. Kirchhoff's Voltage Law:  $\sum V_i = 0$
  8. Conductance:  $G = \frac{1}{R}$
  9. Equivalent resistance:  $R_{eq} = \frac{V_{test}}{I_{test}}$
- ( $R_{eq}$ ) Turn off all independent sources (dependent sources remain unchanged) and calculate the resulting resistance at the desired port. Notice that you may have to apply the i-v test if resistors cannot be combined through series and parallel connections, or if the circuit includes dependent sources.
- ( $V_{th}$ ) Leave the desired port open-circuited (i.e. no load connected) and find the voltage across it.
- ( $I_N$ ) Short-circuit the desired port (i.e. connect a short circuit across the port) and find the current through it.